

Digital Design and Computer Organization Laboratory

UE21CS251A

3rd Semester, Academic Year 2022-23

Date: 27/08/2022

Name: SUJAL S	SRN: PES2UG21CS548	Section I
---------------	-----------------------	--------------

Week# __2__

Program Number : __1__

Title of the Program SIMPLE_CIRCUIT

Aim:

WRITE A VERILOG PROGRAM TO MODEL THE GIVEN SIMPLE CIRCUIT.GENERATE THE VVP OUTPUT AND VIEW THE SIMULATION WAVEFORM USING GTKWAVE.VERIFY THE OUTPUT AND WAVEFORM WITH THE RELEVANT TRUTH TABLE


```
module my_simple_circuit(a,b,c,d,e);  
  
    output d,e;  
    input a,b,c;  
  
    wire w1;  
  
    assign w1 = a & b;  
  
    assign e = ~c ;  
    assign d = e | w1;  
  
endmodule
```

```
C:\iverilog\bin>iverilog.exe -o sujal mysimplecircuit.v simplecircuit_testbench.v
```

```
C:\iverilog\bin>vvp sujal
```

```
UCD info: dumpfile M.ucd opened for output.
```
 
```
0A=0, B=0, C=0, D=1 ,E=1
20A=0, B=0, C=1, D=0 ,E=0
40A=0, B=1, C=0, D=1 ,E=1
60A=0, B=1, C=1, D=0 ,E=0
80A=1, B=0, C=0, D=1 ,E=1
100A=1, B=0, C=1, D=0 ,E=0
120A=1, B=1, C=0, D=1 ,E=1
140A=1, B=1, C=1, D=1 ,E=0
```



a	b	c	d(output)	e(output)
---	---	---	-----------	-----------

0	0	0	1	1
0	0	1	0	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0

Date:27/08/2022

Name: SUJAL S	SRN: PES2UG21CS548	Section I
---------------	-----------------------	--------------

Week# __2__

Program Number: __2__

Title of the Program

CIRCUIT1

Aim:

**WRITE A VERILOG PROGRAM TO MODEL THE GIVEN CIRCUIT1.
GENERATE THE VVP OUTPUT AND VIEW THE SIMULATION
WAVEFORM USING GTKWAVE.VERIFY THE OUTPUT AND
WAVEFORM WITH THE RELEVANT TRUTH TABLE**


```
module my_circuit1(a,b,c,d);  
  
    input a,b,c;  
    output d;  
  
    wire w;  
  
    assign w = c & b;  
    assign d = w | a;  
  
endmodule
```

```
C:\iverilog\bin>iverilog.exe -o answer my_circuit1.v circuit1_testbench.v
```

```
C:\iverilog\bin>vvp answer
```

```
UCD info: dumpfile M1.ucd opened for output.
```
 
```
0A=0, B=0, C=0,Y=0
30A=0, B=0, C=1,Y=0
60A=0, B=1, C=0,Y=0
90A=0, B=1, C=1,Y=1
120A=1, B=0, C=0,Y=1
150A=1, B=0, C=1,Y=1
180A=1, B=1, C=0,Y=1
210A=1, B=1, C=1,Y=1
```



A	B	C	Y(Output)
---	---	---	-----------

0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Date:27/08/2022

Name: SUJAL S	SRN:PES2UG21CS548	Section:I
---------------	-------------------	-----------

Week#__2__

Program Number: __3__

Title of the Program

CIRCUIT2

Aim:

**WRITE A VERILOG PROGRAM TO MODEL THE GIVEN CIRCUIT2.
GENERATE THE VVP OUTPUT AND VIEW THE SIMULATION
WAVEFORM USING GTKWAVE.VERIFY THE OUTPUT AND
WAVEFORM WITH THE RELEVANT TRUTH TABLE**

```
module my_circuit2(A,B,C,Y);  
  
output Y;  
input A,B,C;  
  
wire w1,w2,w3;  
  
assign w1= C & B;  
assign w2= w1 | A;  
assign w3= A & B;  
assign Y = w3 | w2;  
  
endmodule
```

```
C:\iverilog\bin>iverilog.exe -o sujal my_circuit2.v circuit2_testbench.v
```

```
C:\iverilog\bin>vvp sujal
```

```
UCD info: dumpfile M2.vcd opened for output.
```

```
00A=0, B=0, C=0, Y=0
```

```
20A=0, B=0, C=1, Y=0
```

```
40A=0, B=1, C=0, Y=0
```


```
60A=0, B=1, C=1, Y=1
```

```
80A=1, B=0, C=0, Y=1
```

```
100A=1, B=0, C=1, Y=1
```

```
120A=1, B=1, C=0, Y=1
```

```
140A=1, B=1, C=1, Y=1
```

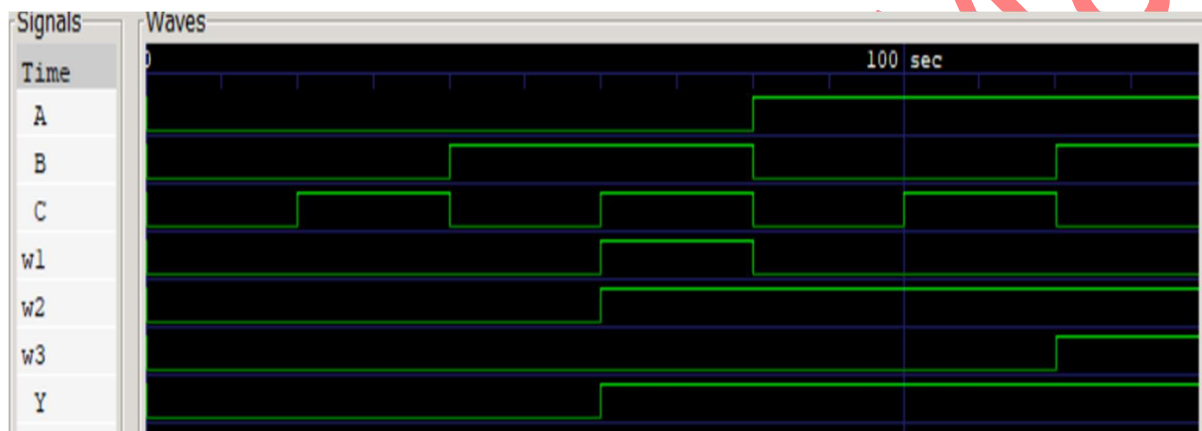

A	B	C	Y(Output)
---	---	---	-----------

0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Date:27/08/2022

Name: SUJAL S	SRN: PES2UG21CS548	Section I
---------------	-----------------------	--------------

Week# __2__

Program Number: __4__

Title of the Program

Half Adder

Aim:

WRITE A VERILOG PROGRAM TO MODEL THE HALF ADDER. GENERATE THE VVP OUTPUT AND VIEW THE SIMULATION WAVEFORM USING GTKWAVE.VERIFY THE OUTPUT AND WAVEFORM WITH THE RELEVANT TRUTH TABLE

```
1  module my_halfadder(a, b, sum, carryout);
2
3  input a,b;
4  output sum,carryout;
5
6  assign sum = a & (~b) | (~a) & b;
7  assign carryout = a & b ;
8
9  endmodule
```

```
C:\iverilog\bin>iverilog.exe -o adder halfadder.v halfadder_testbench.v
```

```
C:\iverilog\bin>vvp adder
```


```
VCD info: dumpfile adder.vcd opened for output.
```

```
0a=0, b=0,sum=0,carry=0
```

```
5a=0, b=1,sum=1,carry=0
```

```
10a=1, b=0,sum=1,carry=0
```

```
15a=1, b=1,sum=0,carry=1
```

 

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Date:27/08/2022

Name: SUJAL S	SRN:PES2UG21CS548	Section I
---------------	-------------------	--------------

Week#__2__

Program Number: __5__

Title of the Program

Full Adder

Aim:

WRITE A VERILOG PROGRAM TO MODEL THE FULL ADDER. GENERATE THE VVP OUTPUT AND VIEW THE SIMULATION WAVEFORM USING GTKWAVE.VERIFY THE OUTPUT AND WAVEFORM WITH THE RELEVANT TRUTH TABLE


```
module my_fulladder(a, b, c_in,sum,carryout);  
  
input a,b,c_in;  
output sum,carryout;  
  
assign sum = (a)^(b)^(c_in);  
assign carryout = (a&b) | (c_in & (a^b));  
  
endmodule
```

```

C:\iverilog\bin>iverilog.exe -o fulladder fulladder.v fulladdertestbench.v

C:\iverilog\bin>vvp fulladder
UCD info: dumpfile adder.vcd opened for output.
      0a=0, b=0, c=0,sum=0,carry=0
      5a=0, b=0, c=1,sum=1,carry=0
     10a=0, b=1, c=0,sum=1,carry=0
     15a=0, b=1, c=1,sum=0,carry=1
     20a=1, b=0, c=0,sum=1,carry=0
     25a=1, b=0, c=1,sum=0,carry=1
     30a=1, b=1, c=0,sum=0,carry=1
     35a=1, b=1, c=1,sum=1,carry=1

```

 

Inputs			Outputs	
A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Disclaimer:

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.
- If found plagiarized, I will abide with the disciplinary action of the University.

Signature: SUJAL S
Name: SUJAL S
SRN: PES2UG21CS548
Section: I
Date: 27/08/2022

PES2UG21CS548