

**ASSIGNMENT 3**  
**Digital Design and Computer Organization**  
**UE21CS251A**  
**3<sup>rd</sup> Semester, Academic Year 2021-22**

Date:18/10/2022

Name: SUJAL.S	SRN:PES2UG21CS548	Section I
---------------	-------------------	--------------

Program Number:\_\_\_1\_\_\_

Title of the Program

**AIM: Write a Verilog code and test bench for 4 bit Binary up counter designed using D Flip Flops**

```
C: > iverilog > bin > counter.v
1  module counter (clock ,reset ,out);
2
3  input clock;
4  input reset;
5  output reg[3:0] out;
6
7  always @ (posedge clock)
8  begin
9      if (! reset)
10         out <= 0;
11     else
12         out <= out + 1;
13 end
14
15 endmodule
```

```

module tb_counter;

reg clk;
reg rstn;
wire [3:0] out;

counter  c0 ( .clock (clk),.reset (rstn),.out (out));
always #5 clk = ~clk;

initial begin
    clk <= 0;
    rstn <= 0;

    $monitor ("Time = %0t  Output = %b", $time, out);
    #20  rstn <= 1;
    $monitor ("Time = %0t  Output = %b", $time, out);
    #80  rstn <= 0;
    $monitor ("Time = %0t  Output = %b", $time, out);
    #50  rstn <= 1;
    $monitor ("Time = %0t  Output = %b", $time, out);
    #50 $finish;
end

initial
begin

$dumpfile("counter.vcd");
$dumpvars(0, tb_counter);


```

```
C:\iverilog\bin>iverilog.exe -o output counter.v counter.tb.v
```

```

C:\iverilog\bin>vvp output
UCD info: dumpfile counter.vcd opened for output.
Time = 0  Output = xxxx
Time = 5  Output = 0000
Time = 20  Output = 0000
Time = 25  Output = 0001
Time = 35  Output = 0010
Time = 45  Output = 0011
Time = 55  Output = 0100
Time = 65  Output = 0101
Time = 75  Output = 0110
Time = 85  Output = 0111
Time = 95  Output = 1000
Time = 100 Output = 1000

```

 

**ASSIGNMENT 3**  
**Digital Design and Computer Organization**

**UE21CS251A**

**3<sup>rd</sup> Semester, Academic Year 2021-22**

Date:18/10/2022

Name: SUJAL.S	SRN:PES2UG21CS548	Section I
---------------	-------------------	--------------

Program Number:\_\_\_2\_\_\_

Title of the Program

**Write a Verilog code and test bench for 4-bit Ring Counter by D flipflop**

```
C: > iverilog > bin > ring.v
1  module ring_counter(Clock,Reset,out);
2
3  input Clock;
4  input Reset;
5
6  output [3:0] out;
7  reg [3:0] Count_temp;
8
9  always @(posedge(Clock))
10 begin
11     if(Reset == 1'b0)
12     begin
13         Count_temp <= 4'b0001;
14     end
15
16     else
17     begin
18         Count_temp <= {Count_temp[2:0],Count_temp[3]};
19     end
20 end
21
22 assign Count_out = Count_temp;
23 endmodule
```

```

ring_counter uut(.Clock(Clock),.Reset(Reset),.out(Count_out));

initial Clock = 1'b1;
always #10 Clock = ~ Clock;

initial
begin
    Clock <= 1'b0;
    Reset <= 1'b1;

    $monitor ("T = %0t out = %b", $time, Count_out);
    repeat (2) @(posedge (Clock));

    Reset <= 1'b0;
    Clock <= 1'b1;
    $monitor ("T = %0t out = %b", $time, Count_out);
    repeat (15) @(posedge (Clock));
    $finish;
end

initial
begin

$dumpfile("ring_counter.vcd");
    $dumpvars(0,tb_ring);

end
endmodule

```

```

C:\iverilog\bin>vvp dsn
VCD info: dumpfile rc_test.vcd opened for output.
      0clk=1,out=1000,reset=1
      5clk=0,out=1000,reset=1
     10clk=1,out=0100,reset=0
     15clk=0,out=0100,reset=0
     20clk=1,out=0010,reset=0
     25clk=0,out=0010,reset=0
     30clk=1,out=0001,reset=0
     35clk=0,out=0001,reset=0
     40clk=1,out=1000,reset=0
     45clk=0,out=1000,reset=0

```



# Digital Design and Computer Organization

UE21CS251A

3<sup>rd</sup> Semester, Academic Year 2021-22

Date:18/10/2022

Name: SUJAL.S	SRN: PES2UG21CS548	Section I
---------------	-----------------------	--------------

Program Number:\_\_\_3\_\_\_

Title of the Program

**Write a Verilog code and test bench for 4-bit Johnson Counter by D flipflop**

```
module JohnSon_Counter #(parameter WIDTH=4)(clock,reset,out);

input clock;
input reset;
output [WIDTH-1 : 0] out;

always @ (posedge clock)
begin
    if (!reset)
        out <= 1;
    else
        begin
            out[WIDTH-1] <= ~out[0];

            for (int i = 0; i < (WIDTH-1); i=i+1)
            begin
                out[i] <= out[i+1];
            end
        end
    end
endmodule
```

```

6  wire [WIDTH-1 : 0] out;
7
8  JohnSon_Counter  u0 (.clock (clk), .reset (rstn), .out(out));
9
10 initial clk = 0;
11 always #10 clk = ~clk;
12
13 initial
14 begin
15
16 {clk, rstn} <= 0;
17
18 $monitor ("Time = %0t  Output = %b", $time, out);
19     repeat (2) @(posedge clk);
20     $monitor ("Time = %0t  Output = %b", $time, out);
21     rstn <= 1;
22     $monitor ("Time = %0t  Output = %b", $time, out);
23     repeat (15) @(posedge clk);
24     $monitor ("Time = %0t  Output = %b", $time, out);
25     $finish;
26 end
27
28 initial
29 begin
30
31 $dumpfile("u0.vcd");
32 $dumpvars(0, tb);
33 end
34 endmodule

```

```
T=0  out=xxxx
T=10 out=0001
T=50 out=0000
T=70 out=1000
T=90 out=1100
T=110 out=1110
T=130 out=1111
T=150 out=0111
T=170 out=0011
T=190 out=0001
T=210 out=0000
T=230 out=1000
T=250 out=1100
T=270 out=1110
T=290 out=1111
T=310 out=0111
```

### **Disclaimer:**

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.
- If found plagiarized, I will abide with the disciplinary action of the University.

Signature: Sujal.S  
Name: Sujal.S  
SRN: PES2UG21CS548  
Section: I  
Date: 18/10/2022