

ASSIGNMENT 3

Digital Design and Computer Organization

UE21CS251A

3rd Semester, Academic Year 2021-22

Date:14/09/2022

Name: Sujal.S	SRN:PES2UG21CS548	Section I
---------------	-------------------	--------------

Program Number: __1__

2:1 MUX

AIM: DESIGN A 2 TO 1 MULTIPLEXER AND VERIFY ITS TRUTH TABLE



```
module mux2_1(y,s,i0,i1);  
  
input s,i0,i1;  
output y;  
  
wire t1,t2;  
  
assign t1 = i0 & (~s);  
assign t2 = s & i1;  
  
assign y = t1 | t2;  
  
endmodule
```

```
C:\iverilog\bin>iverilog.exe -o answer two_1mux.v two_1_tb.v
```

```
C:\iverilog\bin>vvp answer
```

```
VCD info: dumpfile mux2_1test.vcd opened for output.
```
  
```
At time = 5, S=0, A=0, B=0, Output = 0
At time = 10, S=0, A=0, B=1, Output = 0
At time = 15, S=0, A=1, B=0, Output = 1
At time = 20, S=0, A=1, B=1, Output = 1
At time = 25, S=1, A=0, B=0, Output = 0
At time = 30, S=1, A=0, B=1, Output = 1
At time = 35, S=1, A=1, B=0, Output = 0
At time = 40, S=1, A=1, B=1, Output = 1
```



Truth
Table

Inputs			Q
A	I_1	I_0	
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

ASSIGNMENT 3

Digital Design and Computer Organization

UE21CS251A

3rd Semester, Academic Year 2021-22

Date: 14/09/2022

Name: Sujal.S	SRN:PES2UG21CS548	Section I
---------------	-------------------	--------------

Program Number: 2

4_1 MUX

AIM: DESIGN A 4 TO 1 MULTIPLEXER AND VERIFY ITS TRUTH TABLE

```
module mux4_1(i,s1,s0,y);  
  
input [0:3]i;  
input s1,s0;  
output y;  
  
wire w1,w2;  
  
mux2_1 a(w1,s0,i[0],i[1]);  
mux2_1 b(w2,s0,i[2],i[3]);  
  
mux2_1 c(y,s1,w1,w2);  
  
endmodule
```


```
module mux2_1(y,s,i0,i1);  
  
input s,i0,i1;  
output y;  
  
wire t1,t2;  
  
assign t1 = i0 & (~s);  
assign t2 = s & i1;  
  
assign y = t1 | t2;  
  
endmodule
```

```

C:\iverilog\bin>iverilog.exe -o out two_1mux.v 4_1.v 4_1_tb.v


C:\iverilog\bin>vvp out
UCD info: dumpfile mux4_1.vcd opened for output.
At time = 5, Inputs=1000,s1=0,s0=0,Output = 1
At time = 10, Inputs=0100,s1=0,s0=1,Output = 1
At time = 15, Inputs=0010,s1=1,s0=0,Output = 1
At time = 20, Inputs=0001,s1=1,s0=1,Output = 1

```

 

Input	S1	S0	Y
I ₀	0	0	I ₀
I ₁	0	1	I ₁
I ₂	1	0	I ₂
I ₃	1	1	I ₃
 
$$Y = S_1 S_0 I_3 + S_1 \bar{S}_0 I_2 + \bar{S}_1 S_0 I_1 + \bar{S}_1 \bar{S}_0 I_0$$



4 to 1 Multiplexer and its truth table

ASSIGNMENT 3

Digital Design and Computer Organization

UE21CS251A

3rd Semester, Academic Year 2021-22

Date:14/09/2022

Name: Sujal.S	SRN:PES2UG21CS548	Section I
---------------	-------------------	--------------

Program Number: ____3____

Title of the Program

1:4 De-MUX

```
module Demux1_4(Y,in,s);  
  
input [0:1]s;  
input in;  
output [0:3]Y;  
  
assign Y[0] = ~s[0] & (~s[1]) & in;  
assign Y[1] = ~s[0] & s[1] & in;  
assign Y[2] = s[0] & (~s[1]) & in;  
assign Y[3] = s[0] & s[1] & in;  
  
endmodule
```

```
C:\iverilog\bin>iverilog.exe -o out 1_4.v 1_4_tb.v
```

```
C:\iverilog\bin>vvp out
```


```
VCD info: dumpfile demux.vcd opened for output.
```

```

0| Din = 1| S [0] = x| S[1] = x| Y [0] = x| Y [1] = x| Y [2] = x| Y [3] = x
5| Din = 1| S [0] = 0| S[1] = 0| Y [0] = 1| Y [1] = 0| Y [2] = 0| Y [3] = 0
10| Din = 1| S [0] = 0| S[1] = 1| Y [0] = 0| Y [1] = 1| Y [2] = 0| Y [3] = 0
15| Din = 1| S [0] = 1| S[1] = 0| Y [0] = 0| Y [1] = 0| Y [2] = 1| Y [3] = 0
20| Din = 1| S [0] = 1| S[1] = 1| Y [0] = 0| Y [1] = 0| Y [2] = 0| Y [3] = 1

```
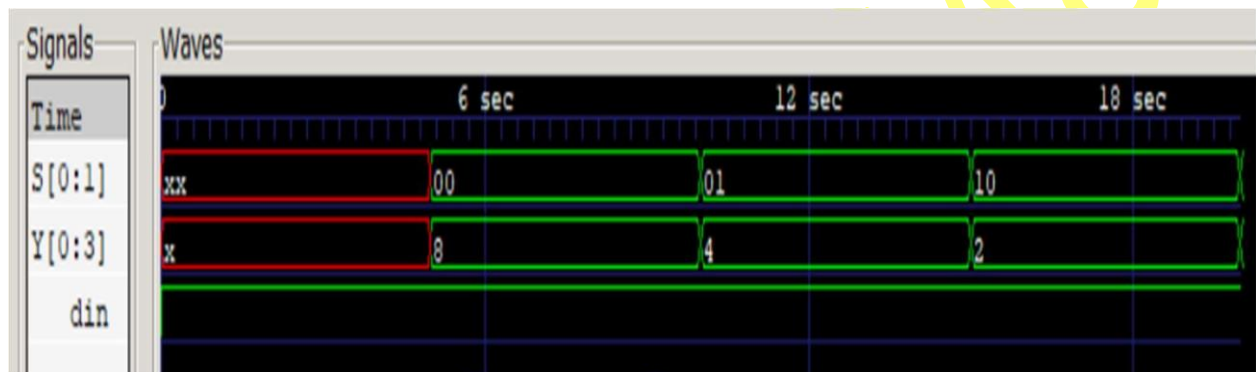
```
C:\iverilog\bin>gtkwave demux.vcd
```



D	S ₁	S ₀	Y ₃	Y ₂	Y ₁	Y ₀
D	0	0	0	0	0	D
D	0	1	0	0	D	0
D	1	0	0	D	0	0
D	1	1	D	0	0	0

Digital Design and Computer Organization

ASSIGNMENT 3 UE21CS251A

3rd Semester, Academic Year 2021-22

Date:14/09/2022

Name: Sujal.S	SRN:PES2UG21CS548	Section I
---------------	-------------------	--------------

Program Number: 4

AIM: DESIGN A 2 TO 4 DECODER AND VERIFY ITS TRUTH TABLE

```
module Decoder2_4(enable,a,b,y);  
  
    input enable,a,b;  
    output [0:3]y;  
  
    wire enb,na,nb;  
  
    assign enb = ~enable;  
    assign na = ~a;  
    assign nb = ~b;  
  
    assign y[0] = na & nb;  
    assign y[1] = na & b;  
    assign y[2] = a & nb;  
    assign y[3] = a & b;  
  
endmodule
```

```
C:\iverilog\bin>iverilog.exe -o out 2_4.v 2_4_tb.v
```

```
C:\iverilog\bin>vvp out
```

```
UCD info: dumpfile Decoder2_4test.vcd opened for output.
```



```
en=1 a=x b=x y=xxxx
```

```
en=0 a=0 b=0 y=1000
```

```
en=0 a=0 b=1 y=0100
```

```
en=0 a=1 b=0 y=0010
```

```
en=0 a=1 b=1 y=0001
```

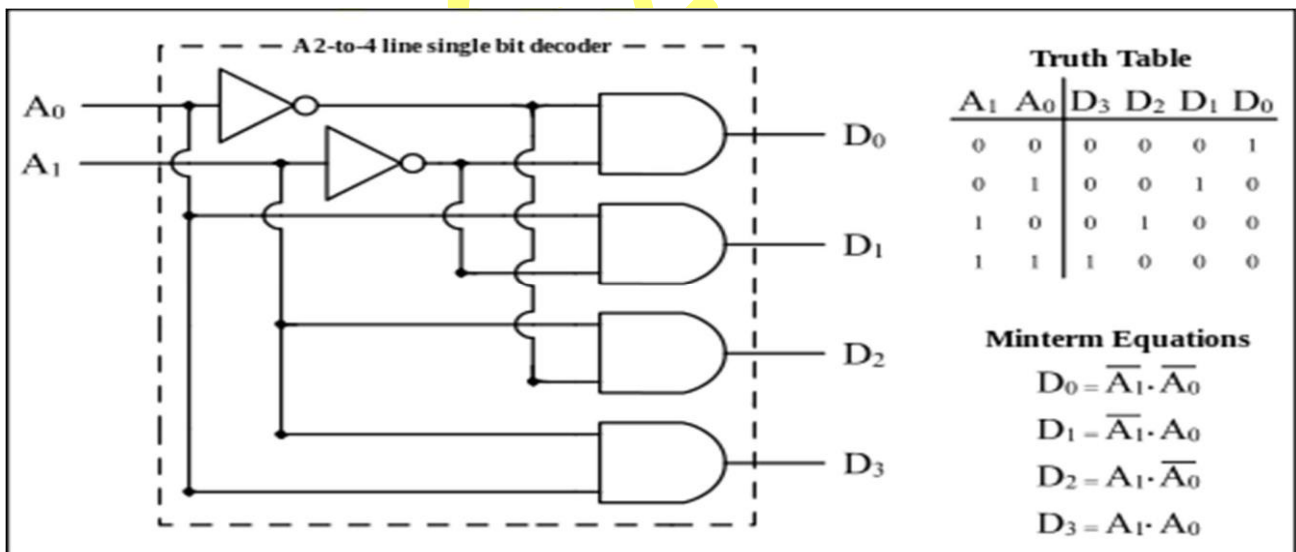 

Disclaimer:

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.
- If found plagiarized, I will abide with the disciplinary action of the University.

Signature: Sujal.S

Name: Sujal.S

SRN:PES2UG21CS548

Section: I

Date:11/09/2022