



**END SEMESTER ASSESSMENT (ESA)**  
**B.TECH. (CSE)**  
**III SEMESTER**

**UE18CS206 – DIGITAL DESIGN & COMPUTER  
ORGANIZATION LABORATORY**

**PROJECT REPORT**  
**ON**

**“4 BIT UP DOWN COUNTER USING  
JK FLIP FLOPS”**

**SUBMITTED BY**

| <b>NAME</b>                     | <b>SRN</b>           |
|---------------------------------|----------------------|
| <b>Student1:SUJAL S</b>         | <b>PES2UG21CS548</b> |
| <b>Student2:SUDHANVA SAMAGA</b> | <b>PES2UG21CS544</b> |
| <b>Student3:SRINIVAASAN N S</b> | <b>PES2UG21CS542</b> |
| <b>Student4:SHREY</b>           | <b>PES2UG21CS500</b> |

**DEPARTMENT OF COMPUTER SCIENCE & ENGINEERING**

**ELECTRONIC CITY CAMPUS,**

**BENGALURU – 560100, KARNATAKA, INDIA**

| TABLE OF CONTENTS |                         |         |
|-------------------|-------------------------|---------|
| Sl.No             | TOPIC                   | PAGE No |
| 1.                | ABSTRACT OF THE PROJECT | 1       |
| 2.                | CIRCUIT DIAGRAM         | 2       |
| 3.                | MAIN VERILOG CODE       | 4       |
| 4.                | TEST BENCH FILE         | 5       |
| 5.                | SCREEN SHOTS            | 6       |

## ABSTRACT OF THE PROJECT:

This project takes us on a tour in which we design a 4bit

Synchronous up down counter using Verilog.

The counter is implemented by the use of 4 jk flip flops since it is a 4 bit counter.

Jk flip flops are different from SR flip flops in the way they toggle while inputs are both 1.

Since it is a synchronous counter there is a single clock to all the 4 flip flops. We have implemented a switch which allows us to toggle between the counters(up and down).


The input being x,output is incremented by 1 in the up counter and is decremented by 1 in the down counter.

The Gtksignal changes with respect to clock input every 5 units of time.



The Output in the up counter is Q whereas in the down counter it is the negation which is Qbar.

## CIRCUIT DIAGRAM:
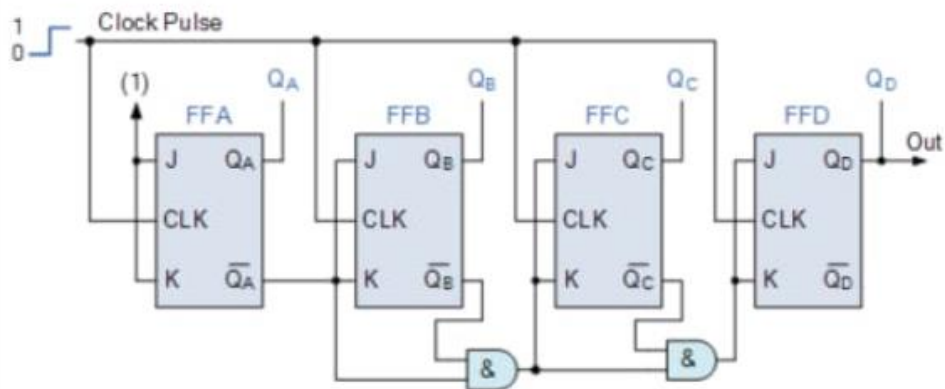
### Binary 4-bit Synchronous Down Counter



### Binary 4-bit Synchronous Up Counter

 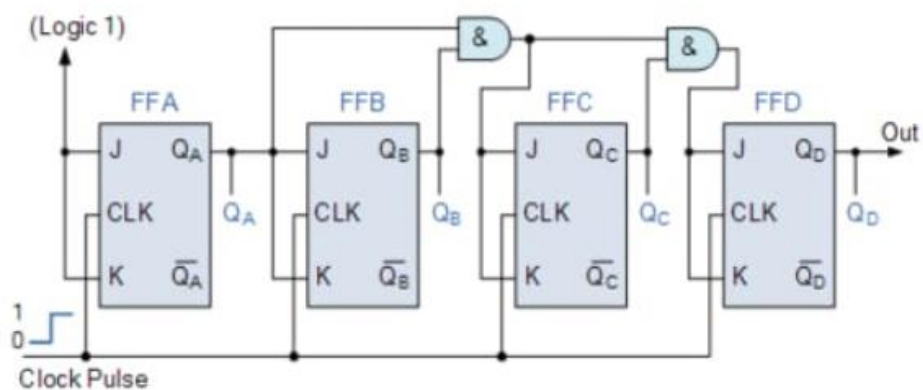

## MAIN VERILOG CODE:

```
`timescale 1ns / 1ps
```

```
module JKFlipFlop(Q,Q_Bar,J,K,Clock,Reset);    // Implementation Of JK Flipflop ..
```

```
input J,K;
```

```
input Clock,Reset;
```

```
output reg Q;
```

```
output reg Q_Bar;
```

```
always @ (posedge Clock)
```

```
begin
```

```
if (Reset == 1'b1)
```

```
begin
```

```
    Q <= 1'b0;
```

```
end
```

```
else
```

```
begin
```

```
    case({J,K})
```

```
        2'b00 : Q <= Q;                // Both J And K == 0 then Memory state..
```

```
        2'b01 : Q <= 1'b0;            // If J = 0; K = 1 then reset state
```

```
        2'b10 : Q <= 1'b1;            // If J = 1; K = 0 then Set state
```

```
        2'b11 : Q <= ~Q;              // Both J And K == 1 then Toggle state..
```

```
    endcase
```

```
end
```

```
Q_Bar <= ~(Q);
```

**end**

**endmodule**

**module UpDownCounter(Switch,Q\_out,Q\_barout,J,K,Clock,Reset);**

**input wire Switch;**

**input wire [3:0]J;**

**input wire [3:0]K;**

**input wire Clock;**

**input wire Reset;**

**output wire [3:0]Q\_out;**

**output wire [3:0]Q\_barout;**

**if(Switch <= 1'b1)       //Upcounter**

**begin**

**assign J[0] = 1'b1;**

**assign K[0] = 1'b1;**

**assign J[1] = Q\_out[0];**

**assign K[1] = Q\_out[0];**

**assign J[2] = Q\_out[0] & Q\_out[1];**

**assign K[2] = Q\_out[0] & Q\_out[1];**

**assign J[3] = Q\_out[0] & Q\_out[1] & Q\_out[2];**

**assign K[3] = Q\_out[0] & Q\_out[1] & Q\_out[2];**

**JKFlipFlop index0(Q\_out[0],Q\_barout[0],J[0], K[0], Clock,Reset); //LSB**

```

JKFlipFlop index1(Q_out[1],Q_barout[1],J[1], K[1], Clock,Reset);
JKFlipFlop index2(Q_out[2],Q_barout[2],J[2], K[2], Clock,Reset);
JKFlipFlop index3(Q_out[3],Q_barout[3],J[3], K[3], Clock,Reset); //MSB
end

else // Down Counter
begin
    assign J[0] = 1'b1;
    assign K[0] = 1'b1;

    assign J[1] = Q_barout[0];
    assign K[1] = Q_barout[0];

    assign J[2] = Q_barout[0] & Q_barout[1];
    assign K[2] = Q_barout[0] & Q_barout[1];

    assign J[3] = Q_barout[0] & Q_barout[1] & Q_barout[2];
    assign K[3] = Q_barout[0] & Q_barout[1] & Q_barout[2];

    JKFlipFlop index5(Q_out[0],Q_barout[0],J[0],K[0], Clock,Reset);
    JKFlipFlop index6(Q_out[1],Q_barout[1],J[1], K[1], Clock,Reset);
    JKFlipFlop index7(Q_out[2],Q_barout[2],J[2], K[2], Clock,Reset);
    JKFlipFlop index8(Q_out[3],Q_barout[3],J[3], K[3], Clock,Reset);
end
endmodule

```

## TEST BENCH FILE:

```
timescale 1ns / 1ps

module tb;

reg clock,reset;          // reg == input
reg [3:0]J;
reg [3:0]K;

reg Switch;

wire [3:0]out;            // wire == output
wire [3:0]outBAR;

UpDownCounter answer(Switch,out,outBAR,J,K,clock,reset);

always @ (*)
begin

#5
    clock <= ~clock;
    J <= J + 1'b1;
    K <= K + 1'b1;

end

initial
begin

    Switch = 1'b1;        // indicating to do Upcounter
    reset = 1'b1;
    clock = 1'b1;
    J = 4'b0000;
    K = 4'b0000;

#5 reset = 1'b0;

end

initial
begin

    Switch = 1'b0;        // indicating to do Downcounter
    reset = 1'b1;
    clock = 1'b1;
    J = 4'b0000;
    K = 4'b0000;
```



```

#170 reset = 1'b0;

end

initial
begin
    $monitor($time,"J = %b,K = %b,clock = %b, %b%b%b%b ,reset =
    %b ",J,K,clock,out[3],out[2],out[1],out[0],reset);
    #160;
    $monitor($time,"J = %b,K = %b,clock = %b, %b%b%b%b
    ,reset = %b
    ",J,K,clock,outBAR[3],outBAR[2],outBAR[1],outBAR[0],reset);
    #160 $finish;
end

initial
begin
    $dumpfile ("answer.vcd");
    $dumpvars (0, tb);
end

endmodule

```

## SCREEN SHOT OF THE OUTPUT:

### 1.vvp output


```
C:\iverilog\bin>iverilog.exe -o Output UpDown.v TestBench.v

C:\iverilog\bin>vvp Output
UCD info: dumpfile answer.ucd opened for output.
    0J = 0000,K = 0000,clock = 1, 0000 ,reset = 1
    5J = 0001,K = 0001,clock = 0, 0000 ,reset = 0
   10J = 0010,K = 0010,clock = 1, 0001 ,reset = 0
   15J = 0011,K = 0011,clock = 0, 0001 ,reset = 0
   20J = 0100,K = 0100,clock = 1, 0010 ,reset = 0
   25J = 0101,K = 0101,clock = 0, 0010 ,reset = 0
   30J = 0110,K = 0110,clock = 1, 0011 ,reset = 0
   35J = 0111,K = 0111,clock = 0, 0011 ,reset = 0
   40J = 1000,K = 1000,clock = 1, 0100 ,reset = 0
   45J = 1001,K = 1001,clock = 0, 0100 ,reset = 0
   50J = 1010,K = 1010,clock = 1, 0101 ,reset = 0
   55J = 1011,K = 1011,clock = 0, 0101 ,reset = 0
   60J = 1100,K = 1100,clock = 1, 0110 ,reset = 0
   65J = 1101,K = 1101,clock = 0, 0110 ,reset = 0
   70J = 1110,K = 1110,clock = 1, 0111 ,reset = 0
   75J = 1111,K = 1111,clock = 0, 0111 ,reset = 0
   80J = 0000,K = 0000,clock = 1, 1000 ,reset = 0
   85J = 0001,K = 0001,clock = 0, 1000 ,reset = 0
   90J = 0010,K = 0010,clock = 1, 1001 ,reset = 0
   95J = 0011,K = 0011,clock = 0, 1001 ,reset = 0
  100J = 0100,K = 0100,clock = 1, 1010 ,reset = 0
  105J = 0101,K = 0101,clock = 0, 1010 ,reset = 0
  110J = 0110,K = 0110,clock = 1, 1011 ,reset = 0
  115J = 0111,K = 0111,clock = 0, 1011 ,reset = 0
  120J = 1000,K = 1000,clock = 1, 1100 ,reset = 0
```

```
  120J = 1000,K = 1000,clock = 1, 1100 ,reset = 0
  125J = 1001,K = 1001,clock = 0, 1100 ,reset = 0
  130J = 1010,K = 1010,clock = 1, 1101 ,reset = 0
  135J = 1011,K = 1011,clock = 0, 1101 ,reset = 0
  140J = 1100,K = 1100,clock = 1, 1110 ,reset = 0
  145J = 1101,K = 1101,clock = 0, 1110 ,reset = 0
  150J = 1110,K = 1110,clock = 1, 1111 ,reset = 0
  155J = 1111,K = 1111,clock = 0, 1111 ,reset = 0
  160J = 0000,K = 0000,clock = 1, 0000 ,reset = 0
  165J = 0001,K = 0001,clock = 0, 0000 ,reset = 0
  170J = 0010,K = 0010,clock = 1, 1111 ,reset = 0
  175J = 0011,K = 0011,clock = 0, 1111 ,reset = 0
  180J = 0100,K = 0100,clock = 1, 1110 ,reset = 0
  185J = 0101,K = 0101,clock = 0, 1110 ,reset = 0
  190J = 0110,K = 0110,clock = 1, 1101 ,reset = 0
  195J = 0111,K = 0111,clock = 0, 1101 ,reset = 0
  200J = 1000,K = 1000,clock = 1, 1100 ,reset = 0
  205J = 1001,K = 1001,clock = 0, 1100 ,reset = 0
  210J = 1010,K = 1010,clock = 1, 1011 ,reset = 0
  215J = 1011,K = 1011,clock = 0, 1011 ,reset = 0
  220J = 1100,K = 1100,clock = 1, 1010 ,reset = 0
  225J = 1101,K = 1101,clock = 0, 1010 ,reset = 0
  230J = 1110,K = 1110,clock = 1, 1001 ,reset = 0
  235J = 1111,K = 1111,clock = 0, 1001 ,reset = 0
  240J = 0000,K = 0000,clock = 1, 1000 ,reset = 0
  245J = 0001,K = 0001,clock = 0, 1000 ,reset = 0
  250J = 0010,K = 0010,clock = 1, 0111 ,reset = 0
```

```
250J = 0010,K = 0010,clock = 1, 0111 ,reset = 0
255J = 0011,K = 0011,clock = 0, 0111 ,reset = 0
260J = 0100,K = 0100,clock = 1, 0110 ,reset = 0
265J = 0101,K = 0101,clock = 0, 0110 ,reset = 0
270J = 0110,K = 0110,clock = 1, 0101 ,reset = 0
275J = 0111,K = 0111,clock = 0, 0101 ,reset = 0
280J = 1000,K = 1000,clock = 1, 0100 ,reset = 0
285J = 1001,K = 1001,clock = 0, 0100 ,reset = 0
290J = 1010,K = 1010,clock = 1, 0011 ,reset = 0
295J = 1011,K = 1011,clock = 0, 0011 ,reset = 0
300J = 1100,K = 1100,clock = 1, 0010 ,reset = 0
305J = 1101,K = 1101,clock = 0, 0010 ,reset = 0
310J = 1110,K = 1110,clock = 1, 0001 ,reset = 0
315J = 1111,K = 1111,clock = 0, 0001 ,reset = 0
320J = 0000,K = 0000,clock = 1, 0000 ,reset = 0
```

1.up counter=out

 

## 2.Down counter=outBAR

