

Digital Design and Computer Organisation Laboratory

UE20CS256

3rd Semester, Academic Year 2022-23

Date: 18-08-2022

Name: Sujal S	SRN: PES2UG21CS548	Section I
---------------	-----------------------	--------------

Week# ____1____

Program Number: ____1____

TITLE :

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT OR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE OR GATE TRUTH TABLE

```
module Or(A,B,C);  
  
input A,B;  
output C;  
  
assign C = A|B ;  
endmodule
```

```
C:\iverilog\bin>iverilog.exe -o ORR or_mine.v and2_tb.v
```

```
C:\iverilog\bin>vvp ORR
```


```
UCD info: dumpfile OR_test.vcd opened for output.
```

```
0a=0, b=0, c=0
```

```
5a=0, b=1, c=1
```

```
15a=1, b=0, c=1
```

```
30a=1, b=1, c=1
```

 

Digital Design and Computer Organisation Laboratory

UE20CS256

3rd Semester, Academic Year 2022-23

Date: 18-08-2022

Name: Sujal S	SRN: PES2UG21CS548	Section I
---------------	-----------------------	--------------

Week# ____1____ Program Number: ____2____

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A NOT GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NOT GATE TRUTH TABLE

```
module Not( c,a );  
input a;  
output c;  
assign c = ~a;  
endmodule
```


```
C:\iverilog\bin>iverilog.exe -o NOTT not_mine.v and2_tb.v
```

```
C:\iverilog\bin>vvp NOTT
```

```
UCD info: dumpfile NOT_test.vcd opened for output.
```

```
0a=0, c=1
```

```
15a=1, c=0
```

 

Digital Design and Computer Organisation Laboratory

UE20CS256

3rd Semester, Academic Year 2022-23

Date: 18-08-2022

Name: Sujal S	SRN: PES2UG21CS548	Section I
---------------	-----------------------	--------------

Week# ____1____ Program Number: ____3____

TITLE :

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT NAND GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NAND GATE TRUTH TABLE

```
module Nand(a,b,c,Y);  
  
input a,b,c;  
output Y;  
  
assign c = a & b;  
  
assign Y = ~c ;  
  
endmodule
```

```
C:\iverilog\bin>iverilog.exe -o NANDD nand_mine.v and2_tb.v
```

```
C:\iverilog\bin>vvp NANDD
```


```
UCD info: dumpfile Nand_test.vcd opened for output.
```

```
0a=0, b=0, Y=1
```

```
100a=0, b=1, Y=1
```

```
200a=1, b=0, Y=1
```

```
300a=1, b=1, Y=x
```

 

Digital Design and Computer Organisation Laboratory

UE20CS256

3rd Semester, Academic Year 2022-23

Date: 18-08-2022

Name: Sujal S	SRN: PES2UG21CS548	Section I
---------------	-----------------------	--------------

Week# ____1____

Program Number: ____4____

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT NOR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NOR GATE TRUTH TABLE

```
1 module Nor(a,b,c,Y);  
2  
3 input a,b,c;  
4 output Y;  
5  
6 assign c = a | b;  
7 assign Y = ~c;  
8  
9 endmodule
```

```
C:\iverilog\bin>iverilog.exe -o norr nor_mine.v and2_tb.v
```

```
C:\iverilog\bin>vvp norr
```

```
UCD info: dumpfile Nor_test.vcd opened for output.
```


```
0a=0, b=0, c=1
```

```
10a=0, b=1, c=0
```

```
30a=1, b=0, c=0
```

```
60a=1, b=1, c=0
```

```
C:\iverilog\bin>
```

 

Digital Design and Computer Organisation Laboratory

UE20CS256

3rd Semester, Academic Year 2022-23

Date: 18-08-2022

Name: Sujal S	SRN: PES2UG21CS548	Section I
---------------	-----------------------	--------------


Week# 1 Program Number: 5

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT XOR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE AND GATE TRUTH TABLE

```
module Xor(a,b,c,d,Y);  
  
input a,b,c,d;  
output Y;  
  
assign c = ~a&b;  
assign d = ~b&a;  
assign Y = c|d;  
  
endmodule
```
 
```
C:\iverilog\bin>vvp xorr
VCD info: dumpfile Xor_test.vcd opened for output.
      0a=0, b=0, c=0
     10a=0, b=1, c=1
     30a=1, b=0, c=1
     60a=1, b=1, c=0
C:\iverilog\bin>
```



Digital Design and Computer Organisation Laboratory

UE20CS256

3rd Semester, Academic Year 2022-23

Date: 18-08-2022

Name: Sujal S	SRN: PES2UG21CS548	Section I
---------------	-----------------------	--------------

Week# ____1____

Program Number: ____6____

TITLE :

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT XNOR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE AND GATE TRUTH TABLE

```
module Xnor( a,b,c,d,Y);  
input a,b,c,d;  
output Y;  
  
assign c = a & b;  
assign d = ~a & ~b;  
assign Y = c | d;  
  
endmodule
```

```
C:\iverilog\bin>iverilog.exe -o xnorr xnor_mine.v and2_tb.v
```

```
C:\iverilog\bin>vvp xnorr
```


```
VCD info: dumpfile Xnor_test.vcd opened for output.
```

```
0a=0, b=0, c=1
```

```
10a=0, b=1, c=0
```

```
30a=1, b=0, c=0
```

```
60a=1, b=1, c=1
```

 

Disclaimer:

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.
- If found plagiarized, I will abide with the disciplinary action of the University.

Signature: Sujal S

Name: Sujal S

SRN: PES2UG21CS548

Section: I

Date: 18-08-2022